
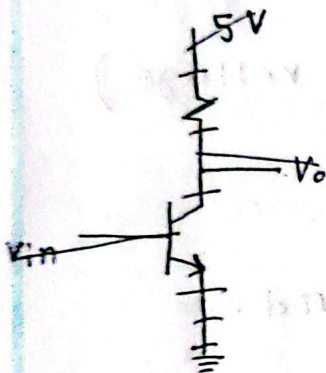
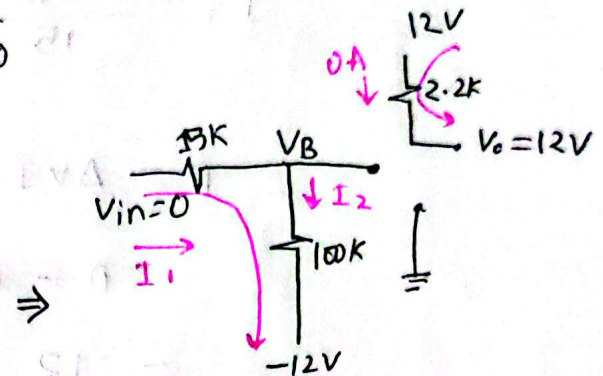


RTL (Resistor Transistor Logic)

RTL Inverter (NOT Gate)

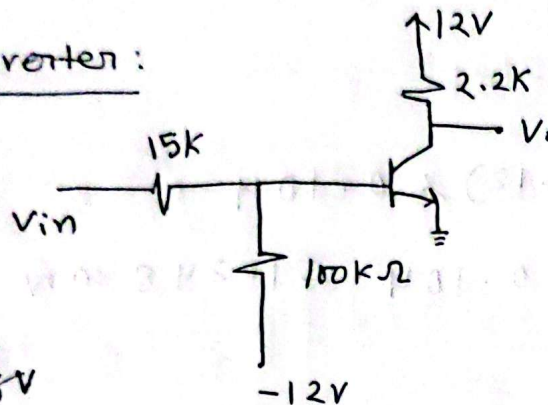

A	$Y = \bar{A}$
0	1
1	0

RTL Inverter:case 1:  $V_{in} = 0V$  (low) $V_o \rightarrow \text{High}$ 

Assume, T is in cutoff mode.

$$I_E = I_B = I_C = 0$$

$$V_{BE} = V_B - V_E = V_B$$

If  $V_{BE} < 0.5V$ ; the T is in cutoff mode.Nodal at  $V_B$ :

$$I_1 = I_2$$

$$\Rightarrow \frac{0 - V_B}{15} = \frac{V_B - (-12)}{100}$$

$$\therefore V_B = -1.56V$$

TOPIC NAME: \_\_\_\_\_

DAY: \_\_\_\_\_

TIME: \_\_\_\_\_

DATE: / /

$$V_{BE} = V_B = -1.56V < 0.5V$$

Assumption correct:

Power dissipation:

$$I_1 = \frac{-V_B}{15} = \frac{-(-1.56)}{15} = 0.104 \text{ mA}$$

$$P = \Delta V I$$

$$= 0 - (-12) \times 0.104$$


$$= 12 \times 0.104 = 1.248 \text{ mW}$$

case 2:  $V_{in} \rightarrow \text{High} = 12V$  (supply voltage) $V_o \rightarrow \text{Low}$ 

Assume, T is in saturation mode.

$$[V_{CE} = 0.2V ; V_{BE} = 0.8V]$$

$$\boxed{\beta_F = 30}$$

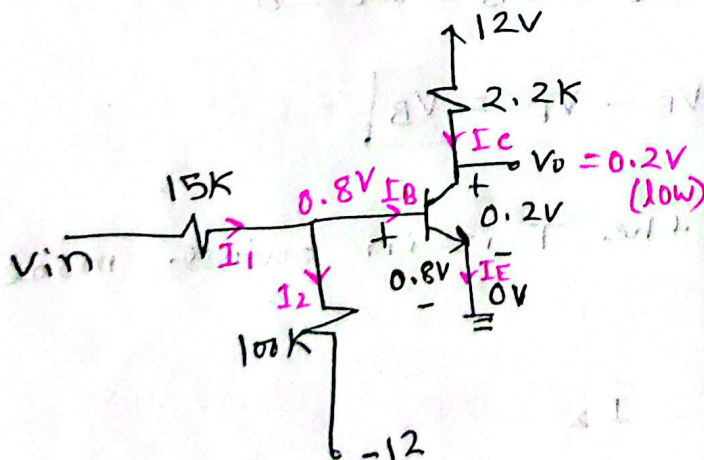

T is in saturation?

calculate  $I_C$ ,  $I_B$ 

$$\text{Then } \beta_{\text{forced}} = \frac{I_C}{I_B}$$

$$\beta_{\text{forced}} < \beta_F \text{ [correct]}$$

$$V_{in} = 12V, V_o = 0.2V$$



$$I_1 = \frac{12 - 0.8}{15} = 0.746 \text{ mA}$$

$$I_2 = \frac{0.8 - (-12)}{100} = 0.128 \text{ mA}$$

$$I_1 = I_2 + I_B$$

$$\therefore I_B = I_1 - I_2 = 0.618 \text{ mA}$$

$$I_C = \frac{12 - 0.2}{2.2} = 5.3636 \text{ mA}$$

$$\beta_{\text{forced}} = \frac{I_C}{I_B} = \frac{5.3636}{0.618} = 8.68 < 30$$

Assumption is correct.

Power dissipation:

$$P = \Delta V I$$

$$= (12 - 0.8) I_1 + [0.8 - (-12)] I_2 + 0.8 I_B \\ + (12 - 0) I_C$$

$$= 74.85 \text{ mW}$$


TOPIC NAME

DAY

TIME

DATE

## RTL Noise Margin

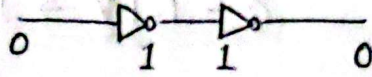


$0-2V \Rightarrow \text{logic } 0$   
 $2V-5V \Rightarrow \text{logic } 1$

O/P of 1st inverter



I/P of the 2nd Inverter

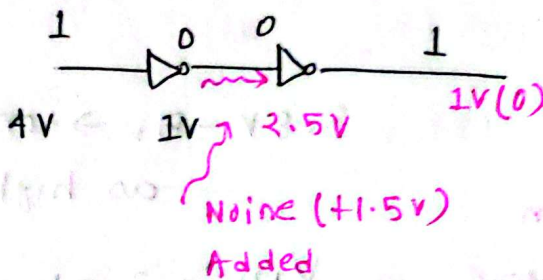


Maximum allowable


noise = 1V

[noise margin]

3.2-5V  $\Rightarrow$  O/P high

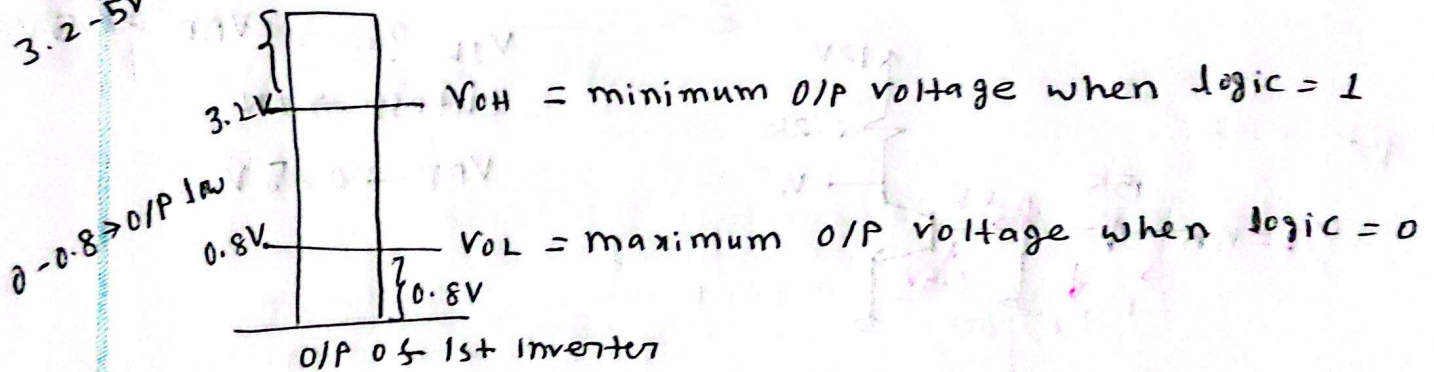

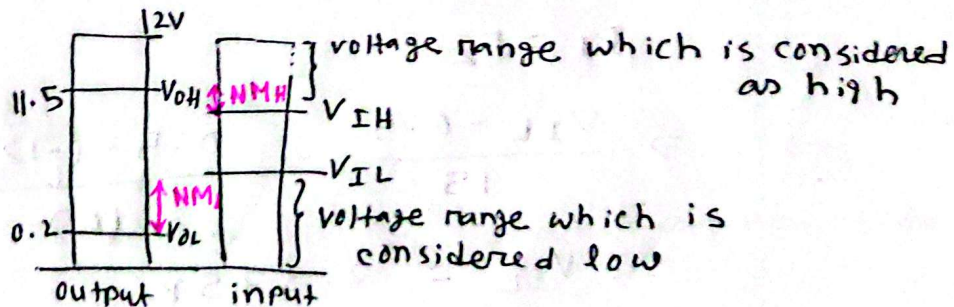$V_{OL} = 0.2V$ ,  $V_{OH} = 11.5V$ , supply voltage = 12V



GOOD LUCK

$V_O = 0.2V$

$V_{in} = 0.2V$

O/P low  $\Rightarrow$  T is in Satn




TOPIC NAME : \_\_\_\_\_

DAY : \_\_\_\_\_

TIME : \_\_\_\_\_


DATE : / /

How do we calculate  $V_{IL}$  = ?

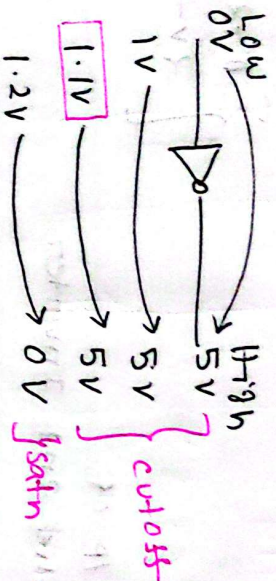


$0 + 1.1V \rightarrow$  low input range

$V_{IL} = 1.1V$

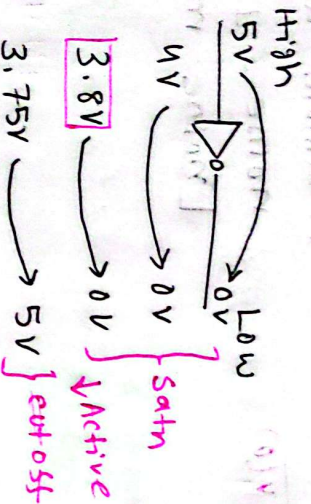

$3.8V - 5V \rightarrow$  considered as high input

$V_{IH} = 3.8V$

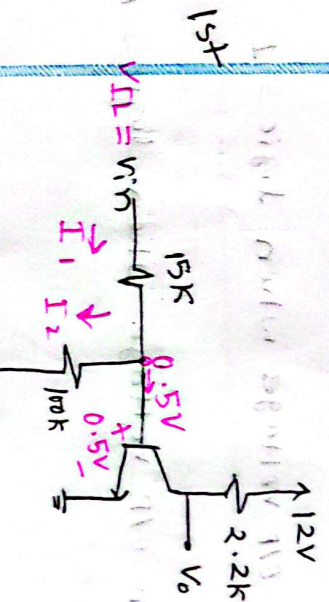

$V_{IL}$  ?  $V_{BE} > 0.5V$

cutoff  $\rightarrow$  AN

$V_{BE} = 0.5V$

GOOD LUCK

$$I_1 = I_2$$

$$\Rightarrow \frac{V_{IL} - 0.5}{15} = \frac{0.5 - (-12)}{100}$$


$$\therefore V_{IL} = 2.375V$$

$(0 - 2.375V) \rightarrow$  considered as logic 0 at the input side

2nd

$$V_{IH} = ?$$

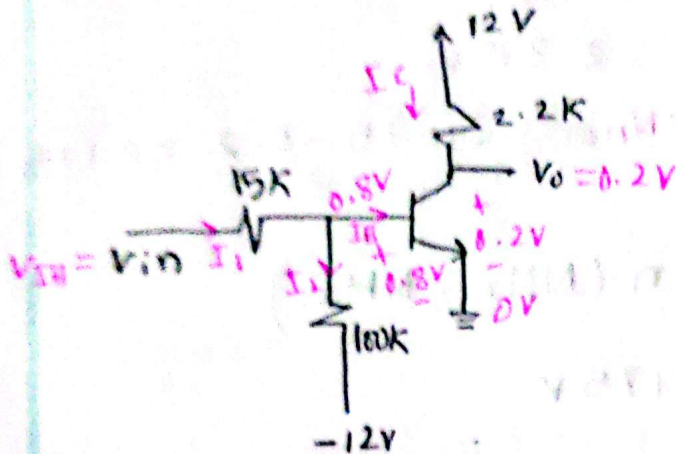↳ Transitioned from saturation to Active mode



$$\beta_{\text{forced}} < \beta_F [\text{satn}]$$

$$\beta_{\text{forced}} > \beta_F [\text{Active}]$$

$$\beta_F = \beta_{\text{forced}} [\text{Transition}]$$

$$I_C = \frac{12 - 0.2}{2.2} = 5.3636 \text{ mA}$$

$$\beta_{\text{forced}} = \frac{I_C}{I_B} = 30$$

$$I_B = \frac{I_C}{30} = 0.178 \text{ mA}$$

$$I_1 = I_2 + I_B$$

$$\Rightarrow \frac{V_{IH} - 0.8}{15} = \frac{0.8 - (-12)}{100} + 0.178$$

$$\Rightarrow V_{IH} = 5.39 \text{ V}$$


5.39V - 12V → considered as logic 1 at input side



TOPIC NAME : \_\_\_\_\_

DAY : \_\_\_\_\_  
TIME : \_\_\_\_\_


DATE: 18 / 2 / 25

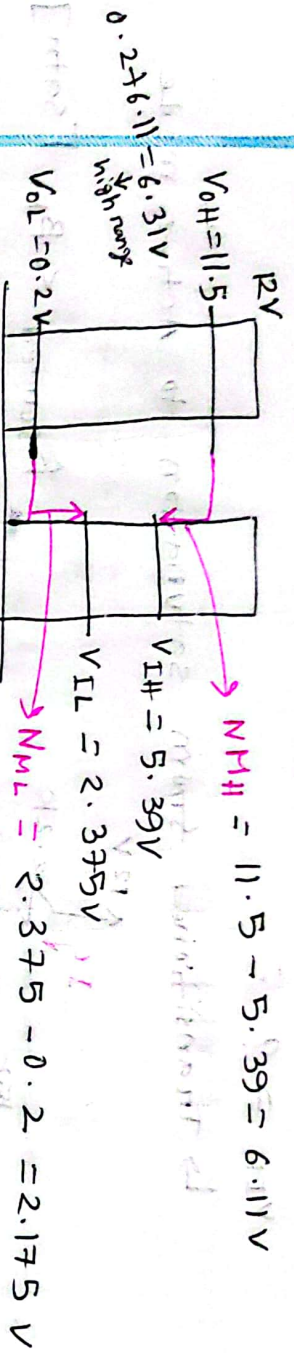


Noise Margin =  $\min(NM_L, NM_H)$

$$= 2.175V$$

### FANOUT

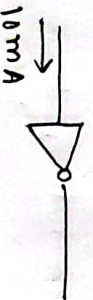

Required current (Properly function)

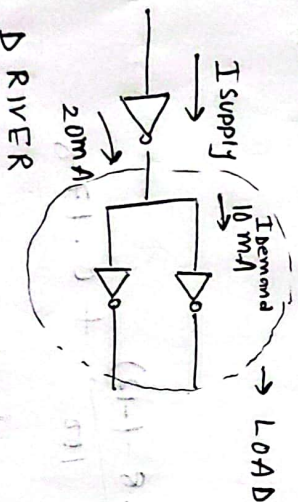

Fanout  $\rightarrow$  maximum no of gate can be connected to the output

$I_{SUPPLY}$  = current supplied by DRIVER

$I_{DEMAND}$  = current required for the load to ...


$$F_{anout} = \frac{I_{SUPPLY}}{I_{DEMAND}}$$

TOPIC NAME : \_\_\_\_\_

DAY : \_\_\_\_\_

TIME : \_\_\_\_\_

DATE : / /

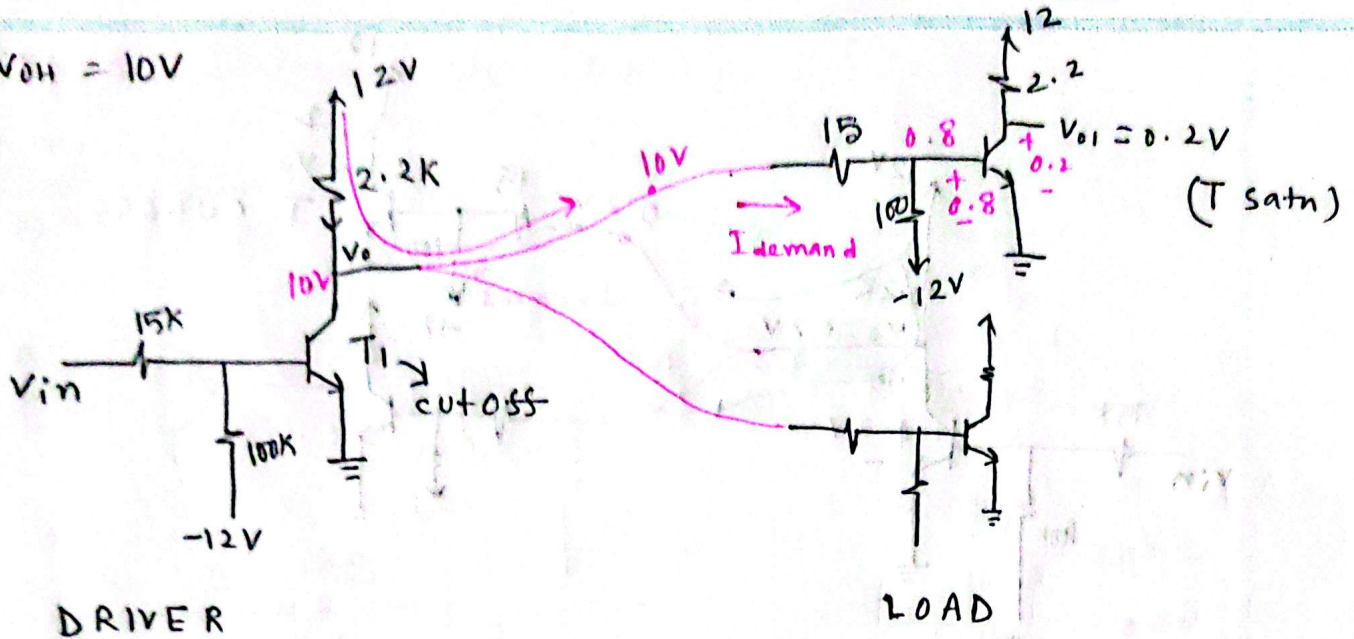 $V_{OH} = 10V$ 

Driver Transistor  $\rightarrow$  cutoff, load circuit transistors  $\rightarrow$  satn

case 01 :  $V_{in} = \text{Low}$  ,  $V_o = 10V$   
 $\rightarrow$  cutoff

$$I_c = \frac{12 - 10}{2.2} = 0.91 \text{ mA} = I_{\text{supply}}$$

$$I_{\text{demand}} = \frac{10 - 0.8}{15} = 0.613 \text{ mA}$$

$$F_{\text{anout}} = \frac{I_{\text{supply}}}{I_{\text{demand}}} = \frac{0.91}{0.613} = (1.43) \times 10^0 = 1$$

\* There would be resistor connected to input terminal and the resistor is connected to the transistor  $\rightarrow$  RTL circuit





case 2

T → saturation

$2.2 \times 10^1$

1115

I demand

$$\text{power} = P_1 + 50 \times P_2$$

$P_2 = \text{load}$        $n$        $n$        $n$