 


## Exercise 1

### Solution:

- a) Assuming High input =  $V_{DD} = 5\text{ V}$  & Low input =  $0\text{ V}$ , we assume,  $D_A$  will be off &  $D_B$  will be on for (1,0).



KCL gives,  $I_{DD} = I_{DA} + I_{DB}$

$$\rightarrow \frac{5-V_O}{R_{DD}} = 0 + \frac{V_O-(V_B+0.7)}{R_B}$$

$$\rightarrow \frac{5-V_O}{100} = \frac{V_O-0-0.7}{1} \rightarrow V_O = 0.743\text{ V}$$

**Verification:** Voltage across  $D_A$ ,  $V_{D_A} = (V_O - I_A \times R_A - V_A)$

$$= (0.743 - 0 - 5) = -4.267 < 0.6\text{ V}$$

Voltage across  $D_B$ ,  $V_{D_B} = 0.7$

Also, the output voltage is lower than that of the high input.

- b) For (0,1),  $D_A$  will be on &  $D_B$  will be off. However, since  $R_A$  &  $R_B$  are same,  $V_O$  will be the same. Now,

$$I_{DD} = I_{DA} + I_{DB} = \frac{V_O - V_A - 0.7}{R_A} + 0 = \frac{0.743 - 0 - 0.7}{1} = 0.043\text{ mA}$$

**Note:** This is also the current that is flowing through  $R_A$ .

- c) Both diodes will be on in this case.

$$\text{So, } I_{DD} = I_{DA} + I_{DB} = \frac{V_O - V_A - 0.7}{R_A} + \frac{V_O - V_B - 0.7}{R_B}$$

$$\rightarrow \frac{V_{DD} - V_O}{R_{DD}} = \frac{V_O - 0 - 0.7}{1} + \frac{V_O - 0 - 0.7}{2} \rightarrow \frac{5 - V_O}{100} = \frac{3(V_O - 0.7)}{2} \rightarrow V_O = 0.728\text{ V}$$

$$\therefore I_{DA} = \frac{V_o - 0.7}{R_A} = \frac{0.728 - 0.7}{1} = 0.028 \text{ mA}$$

$$\therefore I_{DB} = \frac{V_o - 0.7}{R_B} = \frac{0.7228 - 0.7}{2} = 0.014 \text{ mA}$$

d) Voltage of the node between  $D_B$  &  $R_B = V_B + 0.7 = 0 + 0.7 = 0.7 \text{ V}$

## Exercise 2

### Solution:

From **Exercise 1**, we found that the output voltage for (1,0) & (0,1) is 0.743V. The other case when the output voltage will be low is (0,0). For this, KCL gives,

$$I_{DD} = I_{DA} + I_{DB} \rightarrow \frac{V_{DD} - V_o}{R_{DD}} = \frac{V_o - V_A - 0.7}{R_A} + \frac{V_o - V_B - 0.7}{R_B}$$

$$\rightarrow \frac{5 - V_o}{100} = \frac{V_o - 0.7}{1} + \frac{V_o - 0.7}{1} \rightarrow V_o = 0.721 \text{ V}$$

Thus the lower threshold voltage of output for the AND gate =

$$\max(V_{o_{0,0}}, V_{o_{0,1}}, V_{o_{1,0}})$$

$$= \max(0.721, 0.743, 0.743) = 0.743 \text{ V}$$


## Exercise 3

### Solution:

#### Step 1:

Case	DA	DB
0,0	Off	Off
0,1	Off	On
1,0	On	Off
1,1	On	On

(0,0):

 

**Step 2:**

$$I_{DA} = I_{DB} = 0$$

$$\therefore I_o = I_{DA} + I_{DB} = 0$$

$$V_A = V_B = 0.2 \text{ V}$$


Both  $I_{DA}$  &  $I_{DB}$  flows from their respective sources to the ground.

**Step 3:**

$$P = (V_A - 0) \times I_{DA} + (V_B - 0) \times I_{DB}$$

$$\therefore P_{0,0} = (0.2 - 0) \times 0 + (0.2 - 0) \times 0 = 0 \text{ W}$$

(0,1):

 

**Step 2:**

$$I_{DA} = 0, I_{DB} = \frac{V_B - 0.7}{250 + 100 \times 10^3} = \frac{5 - 0.7}{100250} = 42.9 \mu\text{A}$$

$$V_A = 0.2 \text{ V}, V_B = 5 \text{ V}$$


**Step 3:**

$$P = (V_A - 0) \times I_{DA} + (V_B - 0) \times I_{DB}$$

$$\therefore P_{0,1} = (0.2 - 0) \times 0 + (5 - 0) \times 42.9 = 214.5 \mu\text{W}$$

(1,0) can be found similarly. Note that both the diode branches have the same resistances & input voltages. Hence, the result for (1,0) will be the same as (0,1). If those were not the same, the results would differ.

**(1,1):**

 

## Step 2:

$$I_{DA} = I_{DB} = \frac{V_{A-0.7}-V_o}{250}, I_o = I_{DA} + I_{DB} = \frac{V_o-0}{100 \times 10^3}$$

$$\rightarrow 2 \times \frac{V_A - 0.7 - V_o}{250} = \frac{V_o - 0}{100 \times 10^3} \rightarrow V_o = 4.29 V$$

$$\therefore I_{DA} = I_{DB} = \frac{V_o}{100 \times 2} = 21.45 \mu A$$


$$V_A = V_B = 5 \text{ V}$$

### Step 3:

$$P_{1,1} = (5 - 0) \times 21.45 + (5 - 0) \times 21.45 \\ = 214.5 \mu W$$

## Exercise 4

### Solution:

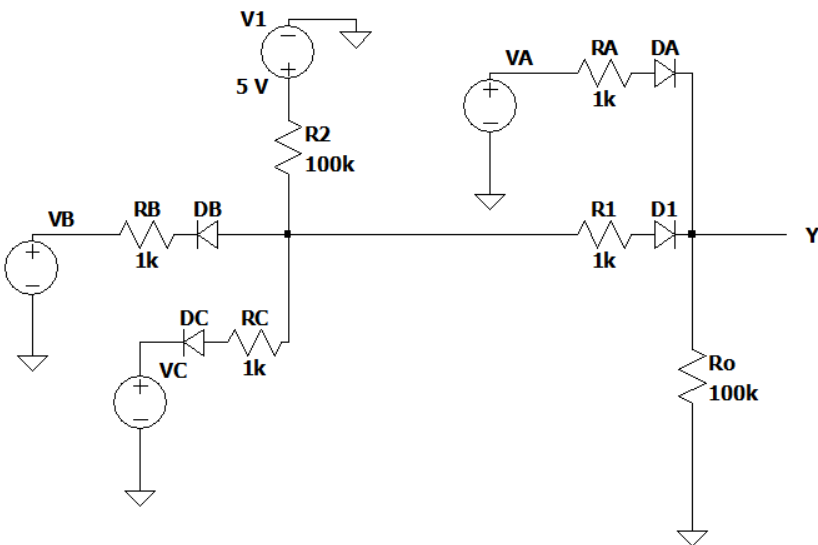

a)  $Y = A + BC$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

b) Output voltage is high for the last 5 rows of input in the truth table.

**Case (0,1,1):**

$D_A, D_B$  &  $D_C$  all are off,  $D_1$  on

Hence, KCL at the output voltage node of the AND gate,  $V_{o(AND)}$  gives,

$$I_{R2} = I_{DB} + I_{DC} + I_{R1} \rightarrow \frac{5-V_{o(AND)}}{100} = 0 + 0 + \frac{V_{o(AND)}-V_Y-0.7}{1}$$

$$\rightarrow 101 V_{o(AND)} - 100V_Y = 75$$

KCL at Y gives,

$$I_{R1} + I_A = I_{R0} \rightarrow \frac{V_{o(AND)}-V_Y-0.7}{1} = \frac{V_Y-0}{100} \rightarrow 100V_{o(AND)} - 101V_Y = 70$$

Solving the two equations,  $V_{o(AND)} = 2.86 V, V_Y = 2.14 V$

**Case (1,0,0):**

$D_A, D_B$  &  $D_C$  all are on,  $D_1$  can be assumed off (since output of AND gate is low)

KCL at AND gate output node,

$$I_{R2} = I_{DB} + I_{DC} \rightarrow \frac{5-V_{o(AND)}}{100} = \frac{V_{o(AND)}-0-0.7}{1} \times 2 \rightarrow V_{o(AND)} = 0.721 V$$

KCL at Y,

$$I_{RA} = I_{R0} \rightarrow \frac{5-V_Y}{1} = \frac{V_Y-0}{100} \rightarrow V_Y = 4.95 V$$

**Case (1,0,1):**

$D_A, D_B$  on,  $D_C$  off,  $D_1$  can be assumed off (since output of AND gate is low)

KCL at AND gate output node,

$$I_{R2} = I_{DB} + I_{DC} \rightarrow \frac{5-V_{o(AND)}}{100} = \frac{V_{o(AND)}-0-0.7}{1} \rightarrow V_{o(AND)} = 0.742 V$$

KCL at Y,

$$I_{RA} = I_{R0} \rightarrow \frac{5-V_Y-0.7}{1} = \frac{V_Y-0}{100} \rightarrow V_Y = 4.25 V$$

**Case (1,1,0):** Same as Case (1,0,1)

**Case (1,1,1):**

*$D_A, D_1$  on, all other diodes are off*

KCL at Y,

$$I_{RA} + I_{R1} = I_{R0} \rightarrow \frac{5-V_Y-0.7}{1} + \frac{5-V_Y-0.7}{101} = \frac{V_Y-0}{100} \rightarrow V_Y = 4.25 V$$

$$\therefore V_{o(AND)} = 5 - I_{R1} \times 100 = 5 - \frac{5-4.94-0.7}{101} \times 100 = 4.96 V$$

Thus, the higher threshold of output voltage =  
 $\min(V_Y \text{ of all high output cases}) = 2.14 V$

Output voltage is low for the first 3 rows of input in the truth table.

**Case (0,0,0):**

*$D_A$  off,  $D_B$  &  $D_C$  on,  $D_1$  can be assumed off*

*(since the output of the AND gate is low)*

KCL at AND gate output node,

$$I_{R2} = I_{DB} + I_{DC} \rightarrow \frac{5-V_{o(AND)}}{100} = \frac{V_{o(AND)}-0-0.7}{1} \times 2 \rightarrow V_{o(AND)} = 0.721 V$$

$V_Y = 0$  (since all diode branches connected to Y are open)

**Case (0,0,1):**

*$D_A$  off,  $D_B$  on,  $D_C$  off,  $D_1$  can be assumed off*

KCL at AND gate output node,

$$I_{R2} = I_{DB} + I_{DC} \rightarrow \frac{5-V_{o(AND)}}{100} = \frac{V_{o(AND)}-0-0.7}{1} \rightarrow V_{o(AND)} = 0.742 V$$

$V_Y = 0$  (for the same reason as previous case)

**Case (0,1,0):** Same as Case (0,0,1)

Thus, lower threshold of output voltage =  $\max(V_Y \text{ of all low output cases})$   
= 0 V

c) Power dissipation of all cases:

**Case (0,0,0):**

$$P_{0,0,0} = (5 - 0) \times I_{R2} = 5 \times \frac{5-0.721}{100} = 0.214 \text{ mW}$$

**Case (0,0,1):**

$$P_{0,0,1} = (5 - 0) \times I_{R2} = 5 \times \frac{5-0.742}{100} = 0.213 \text{ mW}$$

**Case (0,1,0):** Same as Case (0,0,1).

**Case (0,1,1):**

$$P_{0,1,1} = (5 - 0) \times I_{R2} = 5 \times \frac{5-2.86}{100} = 0.107 \text{ mW}$$

**Case (1,0,0):**

$$P_{1,0,0} = (5 - 0) \times I_{R2} + (5 - 0) \times I_{RA} = 5 \times \left( \frac{5-0.721}{100} + \frac{5-4.95}{1} \right) = 0.464 \text{ mW}$$

**Case (1,0,1):**

$$P_{1,0,1} = (5 - 0) \times I_{R2} + (5 - 0) \times I_{RA} = 5 \times \left( \frac{5-0.742}{100} + \frac{5-4.25}{1} \right) = 3.963 \text{ mW}$$

**Case (1,1,0):** Same as Case (1,1,0).

**Case (1,1,1):**

$$P_{1,1,1} = (5 - 0) \times I_{R1} + (5 - 0) \times I_{RA} = 5 \times \left( \frac{4.96-4.25-0.7}{1} + \frac{5-4.25}{1} \right) = 3.8 \text{ mW}$$

$\therefore$  Maximum Power Dissipation,  $P_{max} = 3.8 \text{ mW}$

$$\therefore \text{Average Power Dissipation, } P_{avg} = \frac{0.214 + 0.213 \times 2 + 0.107 + 3.963 + 0.463 \times 2 + 3.8}{8}$$
$$= 1.18 \text{ mW}$$