

Azmari Sultana

Id 22201949

Section 13


Assignment 04

CSE350

①

a2

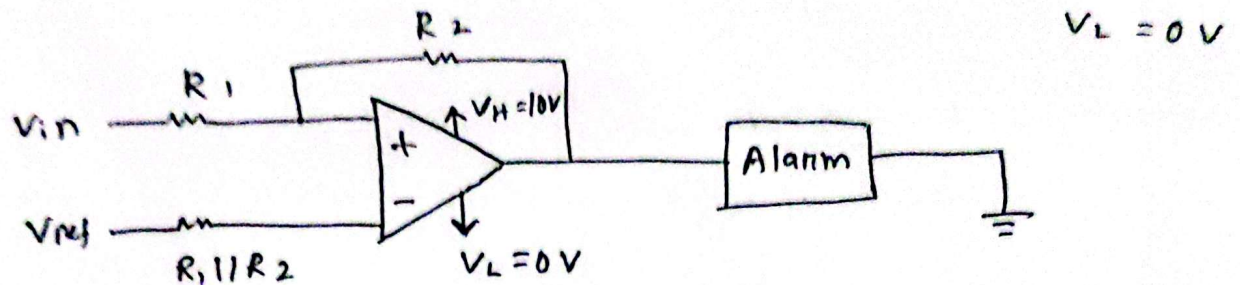The complete circuit of smoke detection and alarm system,



b2

Hence,

for 100% opacity change $\Delta V = 10V$

for 1% " " " $\Delta V = \frac{10}{100} = 0.1V$

$0.1V = 1\% \text{ opacity}$

$\therefore 95\% \text{ opacity} \rightarrow 9.5V$

$$V_{UT} = -\frac{R_1}{R_2} V_L + \frac{R_1 + R_2}{R_2} \cdot V_{ref}$$

$$\Rightarrow 9.5 = -\frac{R_1}{R_2} \times 0 + \frac{R_1 + R_2}{R_2} \times V_{ref}$$

$$\Rightarrow 9.5 = 0 + \left(1 + \frac{R_1}{R_2}\right) V_{ref} \dots (i)$$

$$V_{TL} = -\frac{R_1}{R_2} V_H + \frac{R_1 + R_2}{R_2} V_{ref}$$

$$\Rightarrow 0.5 = -\frac{R_1}{R_2} \times 10 + \left(1 + \frac{R_1}{R_2}\right) V_{ref} \dots (ii)$$

(i) - (ii) :

$$9.5 - 0.5 = \left(1 + \frac{R_1}{R_2}\right) V_{ref} + \frac{R_1}{R_2} \times 10 - \left(1 + \frac{R_1}{R_2}\right) V_{ref}$$

$$\Rightarrow 9 = \frac{R_1}{R_2} \times 10$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{9}{10}$$

$$\therefore R_1 = 9 \text{ k}\Omega$$

$$\therefore R_2 = 10 \text{ k}\Omega$$

Putting the values of R_1 and R_2 in eqn (i) :


$$9.5 = \left(1 + \frac{9}{10}\right) V_{ref}$$

$$\Rightarrow V_{ref} = \frac{95}{19} \text{ V}$$

$$\therefore V_{ref} = 5 \text{ V}$$


(e)

Voltage transfer characteristics curve ,

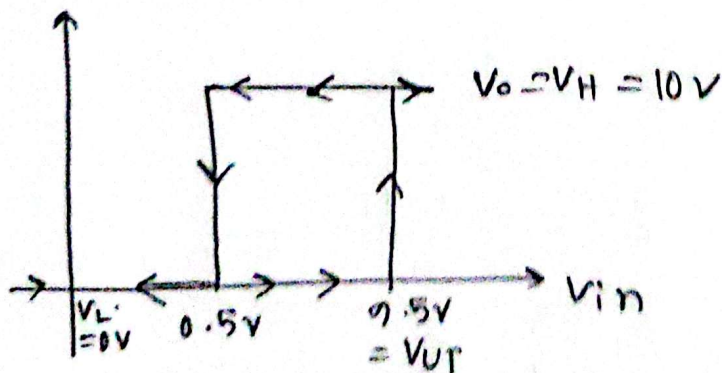

non - inverting

(2)

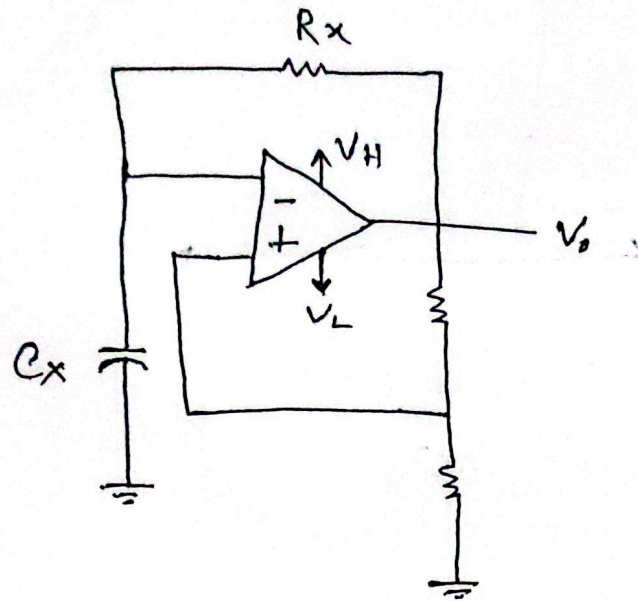(a)(b)

$$V_H = 12V$$

$$V_L = 0V$$

$$\text{Let } R_1 = R_2,$$

$$V_{TH} = \left(\frac{R_1}{R_1 + R_2} \right) V_H = 6V$$


$$V_{TL} = \left(\frac{R_1}{R_1 + R_2} \right) V_L = 0V$$

$$\text{Let, } C_x = 1\mu F$$

$$\therefore R_x = 1.433k\Omega$$

$V_{TL} = V_L$, for this circuit, this will not work properly as square wave generation, this will be high once and again will turn off after 1ms.

(c)

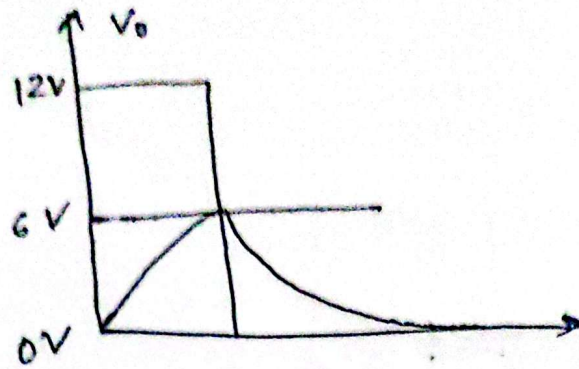

50% of total capacity

Duty cycle = 50%.

$$T_1 = T_2$$

$$T = T_1 + T_2 = T_1 + T_1 = 2T_1$$

$$f = 500 \text{ Hz}$$

$$T = \frac{1}{f} = \frac{1}{500} = 0.002$$

$$\Rightarrow 2T_1 = 2$$

$$\Rightarrow T_1 = 1 \text{ ms}$$

capacitor voltage equation,

$$V_x = V_o + (V_{in} - V_o) e^{-\frac{t_2 - t_1}{R \times C}}$$

$$\Rightarrow 6 = 12 + (0 - 12) e^{-\frac{T_1 - 0}{R \times C}}$$

$$\Rightarrow 0.5 = e^{-\frac{T_1}{R \times C}}$$

$$\Rightarrow T_1 = -R \times C \ln(0.5)$$

$$\therefore R \times C (0.693) = 1 \text{ ms}$$