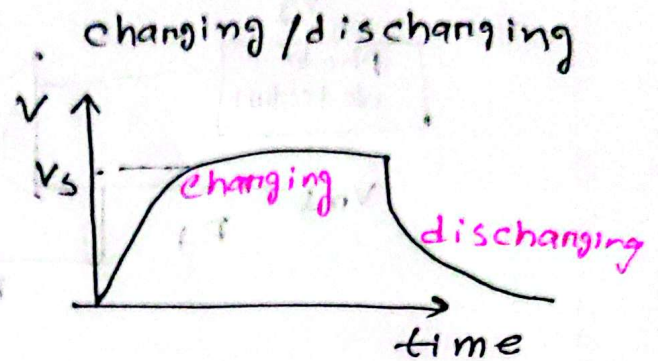
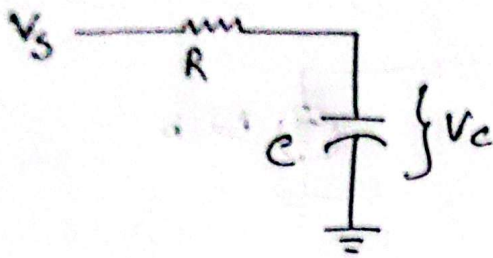


## Square wave generation

Signal Generation

charging  $\Rightarrow V = V_s (1 - e^{-t/RC})$

$$RC = \tau$$

Discharging  $\Rightarrow V = V_s e^{-t/RC}$

$t_1$  = initial time


$t_2$  = final time

$$\begin{aligned}
 V_c(t_2) &= V_c(t_1) e^{-\frac{t_2 - t_1}{RC}} + V_s (1 - e^{-\frac{t_2 - t_1}{RC}}) \\
 &= V_c(t_1) e^{-\frac{t_2 - t_1}{RC}} + V_s (1 - e^{-\frac{t_2 - t_1}{RC}}) \\
 &= V_c(t_1) e^{-\frac{t_2 - t_1}{RC}} + V_s - V_s e^{-\frac{t_2 - t_1}{RC}}
 \end{aligned}$$

$$V_c(t_2) = V_s + (V_c(t_1) - V_s) e^{-\frac{t_2 - t_1}{RC}}$$

$$V_c(t_2) = V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}}) \exp\left(-\frac{t_2 - t_1}{RC}\right)$$

## Square Wave Generator

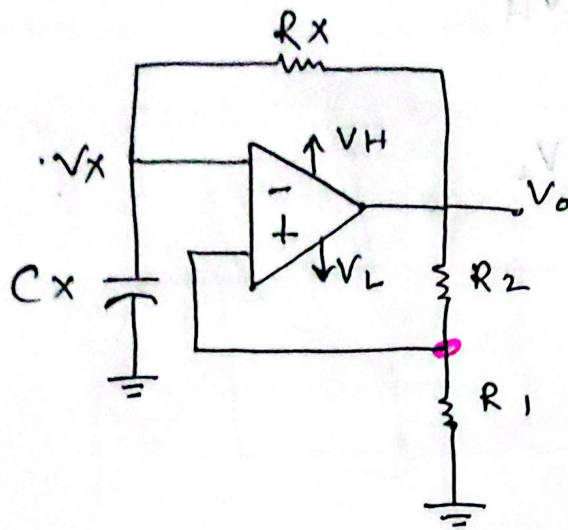


$$V_+ > V_- \rightarrow V_0 = \text{High} = V_H$$

$$V_+ < V_- \rightarrow V_0 = \text{Low} = V_L$$

$$V_H = + \text{ Saturation voltage}$$

$$V_L = - \text{ Saturation voltage}$$

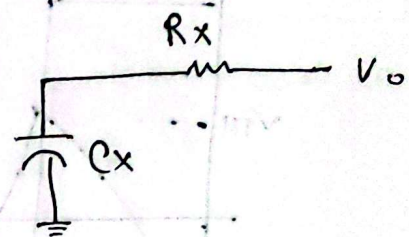

$$V_c(t_2) = V_0 + (V_{\text{initial}} - V_{\text{signal}}) \exp\left(-\frac{t_2 - t_1}{R_x C_x}\right)$$

$$\Rightarrow \frac{V_c(t_2) - V_0}{V_c(t_1) - V_0} = \exp\left(-\frac{t_2 - t_1}{R_x C_x}\right)$$

$$\Rightarrow \ln\left(\frac{V_c(t_2) - V_0}{V_c(t_1) - V_0}\right) = \ln \cdot \exp\left(-\frac{t_2 - t_1}{R_x C_x}\right)$$

$$\Rightarrow t_2 - t_1 = -R_x C_x \ln\left(\frac{V_c(t_2) - V_0}{V_c(t_1) - V_0}\right)$$

$$\Rightarrow t_2 - t_1 = R_x C_x \ln\left(\frac{V_c(t_1) - V_0}{V_c(t_2) - V_0}\right)$$

$$V_0 = V_H \text{ or } V_L$$

$$V_+ = \frac{R_1}{R_1 + R_2} V_H + 0$$


$$V_+ = \frac{R_1}{R_1 + R_2} V_L$$

↑ ground, তাই 0 add, অন্যকিছু থাকলে (পরে add হবে)



$$V_{TH} = \frac{R_1}{R_1 + R_2} V_H$$

$$V_{TL} = \frac{R_1}{R_1 + R_2} V_L$$

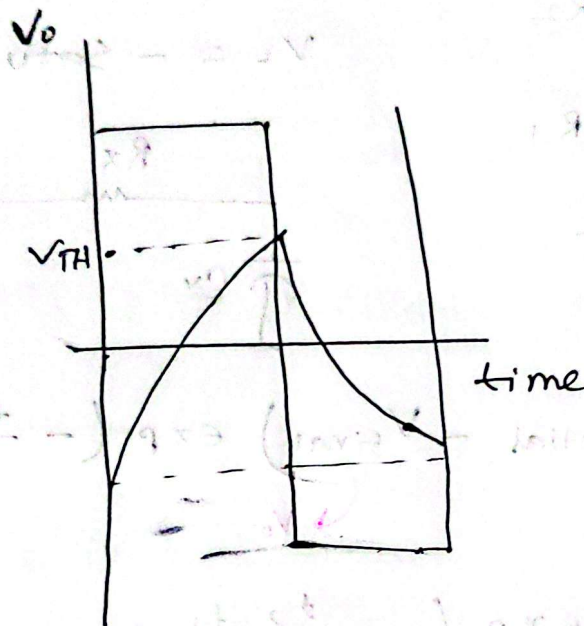

$$V_+ > V_- \Rightarrow V_o = V_H$$

$$\frac{R_1}{R_1 + R_2} V_H > V_x$$


$$V_{TH} < V_x \rightarrow \text{output shift}$$

$$V_- > V_+ \Rightarrow V_o = V_L$$

$$V_x > V_{TL} \rightarrow \frac{R_1}{R_1 + R_2} V_L$$

$$\hookrightarrow V_x < V_{TL}$$

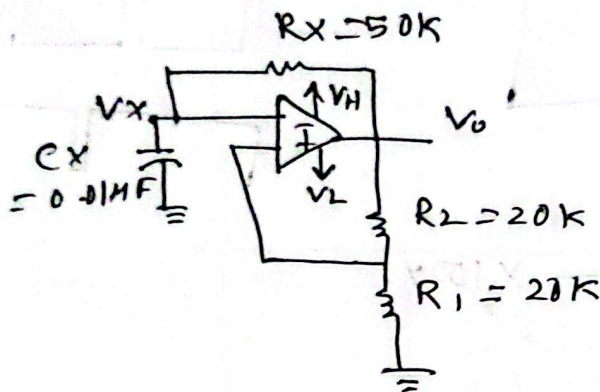\* For the Schmitt-Trigger Oscillator, the saturation output voltages are  $+10\text{V}$  and  $-5\text{V}$ .  $R_1 = R_2 = 20\text{k}\Omega$ ,  $R_x = 50\text{k}\Omega$ ,  $C_x = 0.01\mu\text{F}$ . Determine the frequency of oscillation and duty cycle.



$$V_{TH} = \frac{V_H R_1}{R_1 + R_2} = \frac{10 \times 20}{20 + 20} = 5\text{V}$$

$$V_{TL} = \frac{V_L R_1}{R_1 + R_2} = \frac{-5 \times 20}{20 + 20} = -2.5\text{V}$$

$$\tau = R_x C_x = 50 \times 10^3 \times 0.01 \times 10^{-6} = 0.5\text{ms}$$

$T_1$  = voltage high time duration.

$$= \tau \ln \left( \frac{V_H - V_{TL}}{V_H - V_{TH}} \right)$$

$$= 0.5 \ln \left( \frac{10 - (-2.5)}{10 - 5} \right) = 0.5 \ln(2.5)$$

$T_2$  = voltage low time duration.

$$= \tau \ln \left( \frac{V_L - V_{TH}}{V_L - V_{TL}} \right)$$



$$= 0.5 \ln \left( \frac{-5 - 5}{-5 - 2.5} \right) = 0.5 \ln 4$$

$$\text{Total period, } T = T_1 + T_2 = 0.5 \ln(2.5 \times 4) \\ = 0.5 \ln(10)$$

$$\text{Frequency} = \frac{1}{T} = \frac{1}{0.5 \ln(10)} = 868 \text{ Hz}$$

Duty cycle = % of time voltage is high

$$\Rightarrow \frac{T_1}{T} \times 100\% = \frac{\ln 2.5}{\ln 10} \times 100\%$$

$$= 39.1\%$$

### Triangular Wave Generation


Integration:

$$I_C = C \frac{dV_C}{dt} = \frac{0 - V_S}{R_i}$$


$$\Rightarrow \int_{V_{\text{initial}}} \frac{dV_C}{V_C} = - \int_{t_1}^t \frac{dt}{R_i C}$$

$$\Rightarrow \frac{V_C(t) - V_{\text{initial}}}{V_S} = - \frac{t - t_1}{R_i C}$$
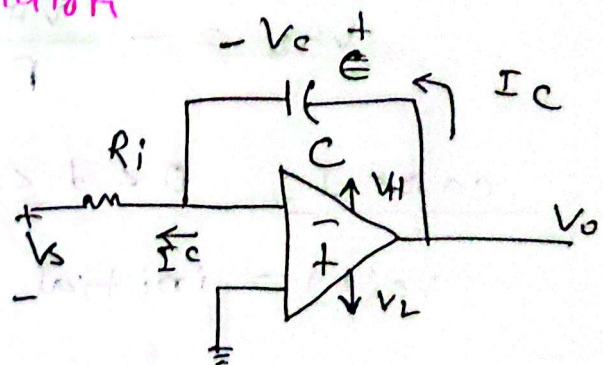
$$V_C(t) = V_{\text{initial}} - \frac{V_S}{R_i C} (t - t_1)$$



## Circuit of Triangular wave generator.

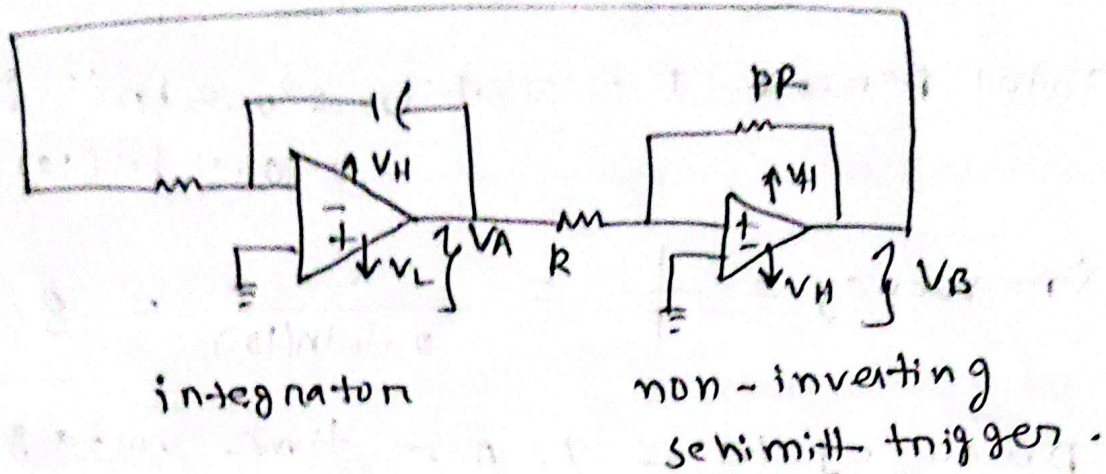


### Triangular wave

$$V_{TH} = - \left( \frac{R}{P \cdot R} \right) V_L$$

$$\Rightarrow V_{TH} = - \frac{V_L}{P}$$

$$V_{TL} = - \frac{V_H}{P}$$

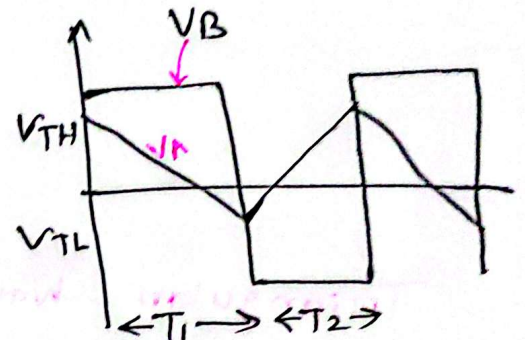

case 1:  $0 < t < T$

$$v_c(t) = \text{initial} - \frac{V_s}{R_{ic}} (t - 0)$$

$$V_c(T_1) = V_{TL} \text{ and } V_c(0) = V_{TH}$$

$$V_c(T_1) = V_{TL}, V_{\text{initial}} = V_{TH}$$

$$T_1 = (R_{ic}) \left( \frac{V_{TH} - V_{TL}}{V_H} \right)$$



$$T_2 = R_i C \cdot \frac{V_{TL} - V_{TH}}{V_L}$$

Therefore, total time period becomes

$$T = T_1 + T_2$$

$$T = \left( \frac{V_{TH} - V_{TL}}{V_H} + \frac{V_{TL} - V_{TH}}{V_L} \right) \times R_i C$$

$$f = \frac{1}{T} \quad \text{Suppose } \left[ V_H = -V_L \text{ and } V_{TH} = -\frac{V_L}{P} \right]$$

$$V_{TL} = -\frac{V_H}{P}$$

$$f = \frac{P}{4 R_i C}$$

# Unipolar triangular wave generation.

(same circuit, only add a diode)

$$f = \frac{P}{2 R_i C}$$

