

TOPIC NAME : _____

DAY : _____


TIME : _____ DATE : / /

Diode Logic (DL): (AND, OR)

OR Gate

logic 0 (0 - 0.8v)

logic 1 (2 - 5v)

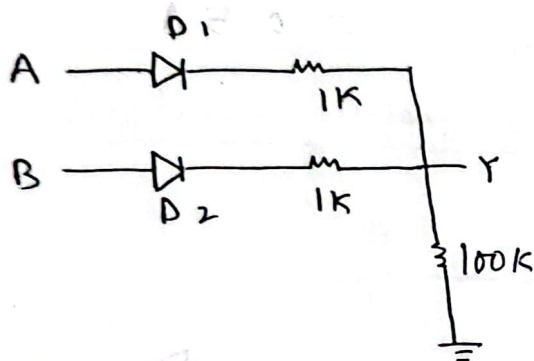


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1 (5v)

Case 1 : (0, 0)

$$V_A = 0V$$

$$V_B = 0V$$

$$D_1, D_2 \rightarrow \text{OFF}$$

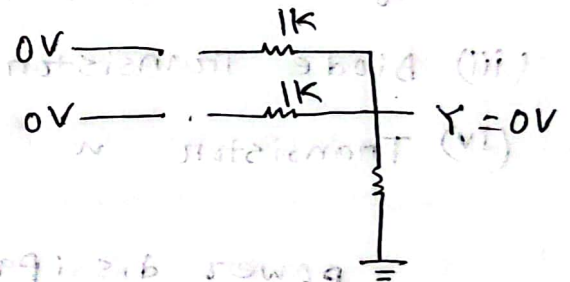

V_A	V_B	V_o
0V	0V	0V
5V	0V	4.25V
0V	5V	4.25V
5V	5V	4.28V

TOPIC NAME: _____

DAY: _____

TIME: _____


DATE: / /

case -02 : (1, 0)

$$V_A = 5V$$

$$V_B = 0V$$

Assume, logic 1 = 5V
logic 0 = 0V

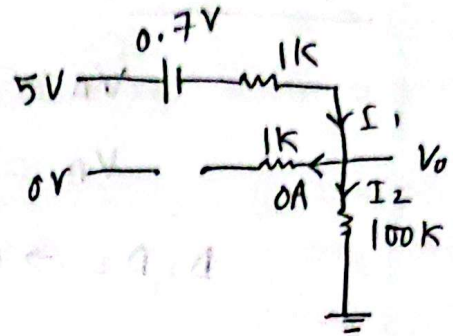
 $D_1 \rightarrow \text{on}$
 $D_2 \rightarrow \text{off}$

Apply nodal at V_0 ,

$$I_1 = I_2$$

$$\Rightarrow \frac{5 - V_0 - 0.7}{1} = \frac{V_0}{100}$$

$$\therefore V_0 = 4.25V$$

$$I_1 = \frac{5 - 4.25 - 0.7}{1}$$

$$= 0.05 \text{ mA}$$

$$I_2 = \frac{4.25}{100}$$

$$= 0.0425 \text{ mA}$$


$$P_{\text{dis}} = I_1^2(1) + I_2^2(100) + 0.7 I_1$$

$$= 0.218 \text{ mW}$$

case 3 : (0, 1)

$$V_A = 0V$$

$$V_B = 5V$$

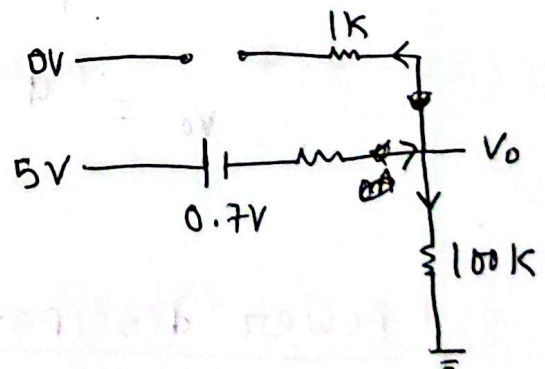 $D_1 \text{ off}, D_2 \text{ on}$


$$\therefore V_0 = 4.25V$$

$$P_{\text{dis}} = 0.218 \text{ mW}$$

case 4 : (1,1)

$$V_A = 5V$$


$$V_B = 5V$$

$$D_1, D_2 \rightarrow \text{on}$$

$$I_1 = \frac{5 - V_0 - 0.7}{1} = \frac{5 - 4.98}{1} = 0.02 \text{ mA}$$

$$I_2 = \frac{5 - V_0 - 0.7}{1} = 0.02 \text{ mA}$$


$$I_3 = \frac{V_0}{100} = 0.0428 \text{ mA}$$

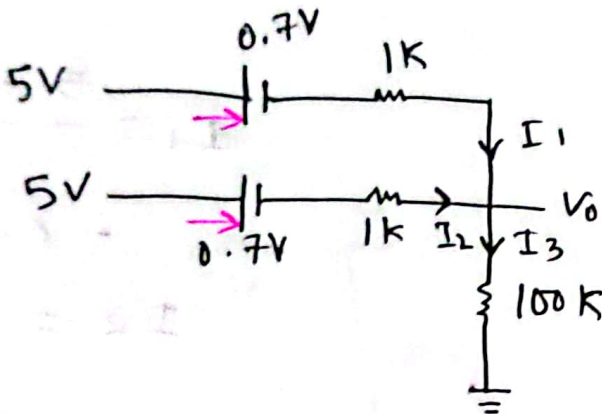Apply node at V_0 ,


$$I_1 + I_2 = I_3$$

$$\Rightarrow \frac{5 - V_0 - 0.7}{1} + \frac{5 - V_0 - 0.7}{1} = \frac{V_0}{100}$$


$$\therefore V_0 = 4.28 \text{ V}$$

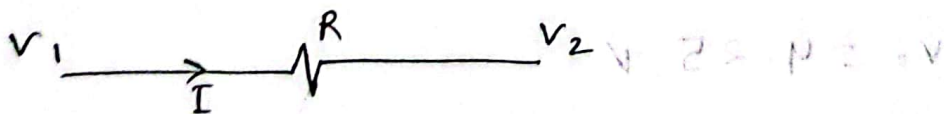Power dissipation:
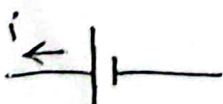
$$P = I^2 R = \Delta V I = (V_1 - V_2) I$$



power supply

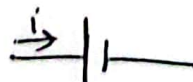

power dissipate

(if i enter in positive side, powerdissi)

TOPIC NAME: _____

DAY: _____

TIME: _____

DATE: / /

Case 4 $I \rightarrow \text{mA}$ $R \rightarrow \text{k}\Omega$ $P \rightarrow \text{mW}$

$$P_{\text{dis}} = I_1^2(1) + I_2^2(1) + I_3^2(100)$$

$$+ 0.7 I_1 + 0.7 I_2$$

$$= 0.211984 \text{ mW}$$

{ dissipate
 শক্তি আছে
 $0.7 I_1 + 0.7 I_2$
 আছে।
 supply শক্তি
 কিছু add করতে

Alternative

$$P = \Delta V I = (5 - 4.28) \times 0.02$$

$$+ (5 - 4.28) \times 0.02$$


$$+ (4.28 - 0) \times 0.0428$$

$$= 0.211984 \text{ mW}$$

যখন V_1 এবং V_2 এর মধ্যস্থিত

same I হয়, তখন এই approach


use করা যাবে।

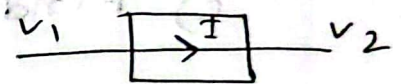

$$P = (V_1 - V_2) I$$

V_A	V_B	V_0	P_{dis}
0V	0V	0	0
5	0	4.25	0.218
0	5	4.25	0.218
5V	5V	4.28V	0.212mW

Q | Mid Fall 24

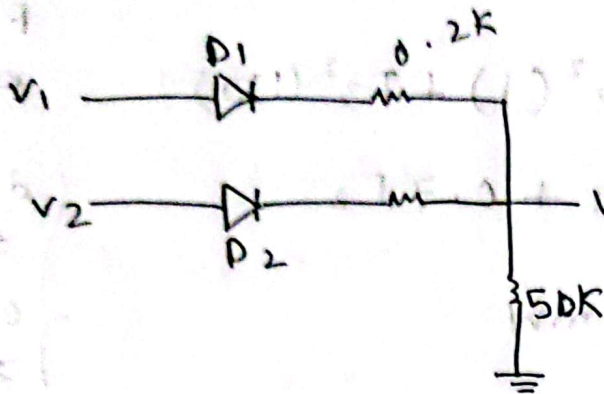

$$\begin{cases} P_2 = P_3 \\ \therefore V_{02} = V_{03} \end{cases}$$

- a) Find the output voltage for the input combination $(V_1=0, V_2=1)$ and $(V_1=0, V_2=0)$.
- b) Which combination of inputs will show maximum power dissipation.
- c) Find average power dissipation.


$$P_{avg} = \frac{P_1 + P_2 + P_3 + P_4}{4}$$

TOPIC NAME: _____

DAY: _____

TIME: _____

DATE: / /

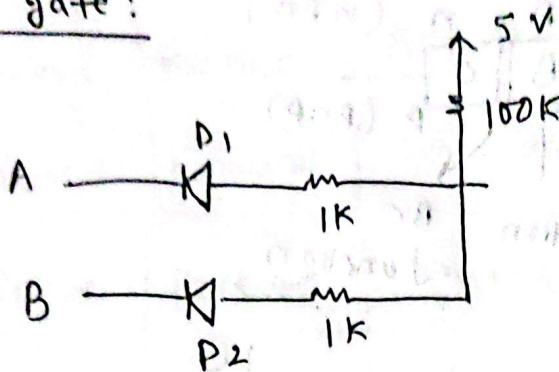Diode LogicAND gate:

$$\text{Logic 1} = 5V$$

$$\text{Logic 0} = 0.2V$$

$$V_D = 0.7V$$

- (i) Find output voltage for all input combination
- (ii) Find power dissipation in the circuit?
- (iii) Is it an AND or OR Gate? Describe?

(brownt) $V_{F.D} < 5V \rightarrow 0.2V$
 (brown) $V_{F.D} > 5V \rightarrow 5V$