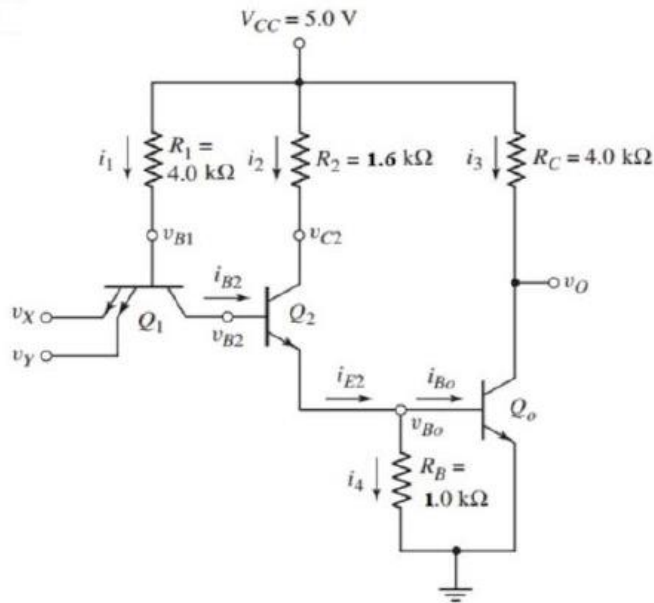


Exercise 1



For the TTL NAND circuit, assume $\beta_F = 25$, $\beta_R = 0.1$

$V_{OH} = 3.4\text{ V}$, $V_{OL} = 0.1\text{ V}$

For saturation mode, assume, $V_{CE} = 0.1\text{ V}$


- Assume no loads are connected to the driver device. If at least one input is low (0.1 V), find i_1 , i_{B2} , i_{Bo} , i_3 .
- Repeat the calculation of (a) if both inputs are high ($v_x = v_y = 5\text{ V}$).
- Find the maximum possible fanout if the loads are also this TTL NAND gate.
- Assume all inputs of the **driver** are **high**.
 - Find the maximum fanout if the other input of the **load** $v_y = 5\text{ V}$ (**High**).
 - If **both inputs** of the **load circuits** are **low**, then what would be the maximum fanout?

Comment and compare on the above two cases to identify which case has better fanout and why?

- Find the power dissipation for all cases [Assume 4 loads are connected to the driver's output]

Ans: a) 1.025 mA , all other currents 0 mA
 b) 0.675 mA , 0.81 mA , 2.5725 mA , 1.225 mA
 c) 5
 d) 1.61 , 2.123
 e) 23.397 mW

Practice Problem 1

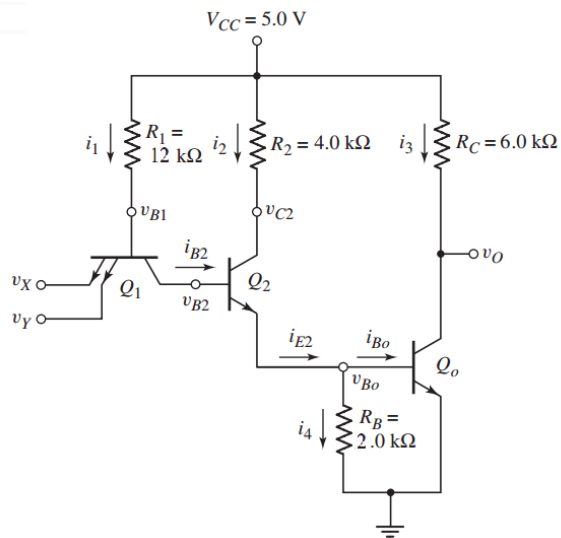

For the given TTL circuit, $\beta_F = 25$, $\beta_R = 0.1$. Assume any of the input to the driver is low and loads are not connected.

- Find i_1 .
- Find i_{B2} .
- Find i_2 .
- Find i_{B0} .
- Find i_3 .

Ans: a) 0.342 mA

b) 0 mA

c) 0 mA


d) 0 mA

e) 0 mA

Now consider all input voltages high, find the same current values again.

Ans: a) 0.225
b) 0.27
c) 1.025
d) 0.895
e) 0.8167

Exercise 2

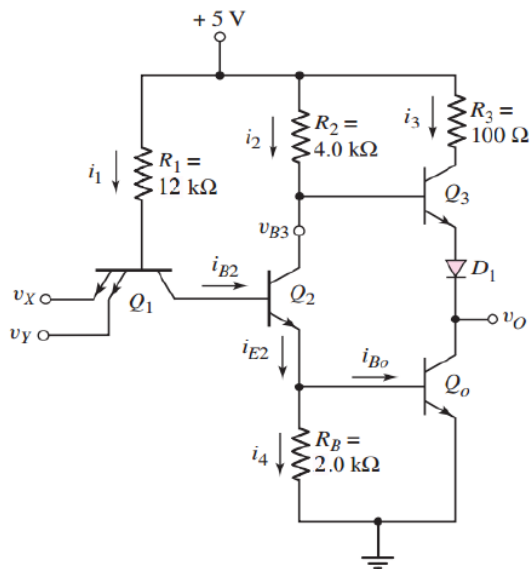


For the given TTL circuit with totem-pole output, assume common emitter current gain, $\beta_F = 25$ and reverse common emitter current gain of the transistors $\beta_R = 0.1$.

- Find the value of β_{min} for transistor Q, so that Q, can remain in saturation when both inputs are high.
- Assume inputs of the load devices are not connected to driver device. If at least one input (0.1 V), find i_1 , i_{B2} , i_2 , i_{Bo} , and i_3 .
- Repeat the calculation of (b) if both the inputs are high ($v_x = v_y = 3.6$ V)
- Find the maximum fanout of this TTL circuit for the case mentioned in (c).
- Find out the maximum power dissipation of the TTL circuit for the case mentioned in (c).
- Calculate maximum fanout for $v_x = v_y = 0.1$ V. Given that $v_o(\text{No load}) = 3.5$ V. And, from this calculation prove that T_4 is in **forward active mode**.

Ans: a) 3.796
 b) 0.3416 mA, 0, 0, 0, 0 mA
 c) 0.2225 mA, 0.27 mA, 0.895 mA, 0 mA
 e) 6.412 mW
 f) 28

Exercise 3

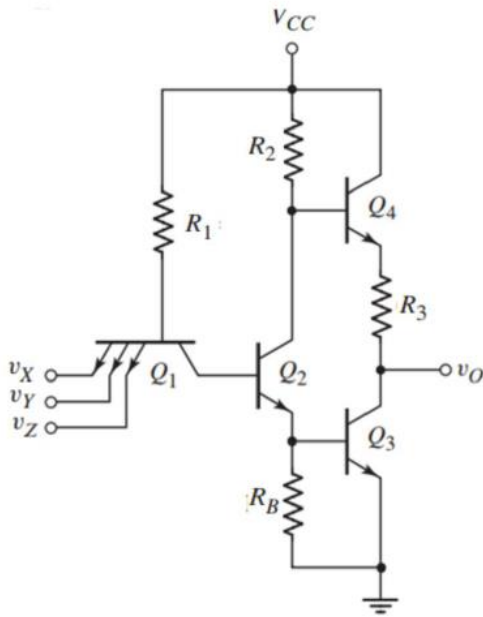

For the given TTL circuit, given

$$R_1 = 3 \text{ k}\Omega, R_2 = 1.3 \text{ k}\Omega,$$

$$R_3 = 0.55 \text{ k}\Omega, \text{ and } R_B = 8 \text{ k}\Omega.$$

Assume $V_{CC} = 3.5 \text{ V}$, common emitter current gain, $\beta_F = 15$ and reverse common emitter current gain of the transistors, $\beta_R = 0.8$.

- If all inputs are high ($v_x = v_y = v_z = 3.5 \text{ V}$), find $i_{B_1}, i_{B_2}, i_{B_3}, i_{B_4}$, and i_{E_3} .
- Assume inputs of the load devices are not connected to the driver device. If at least one input is low (0.1 V), find $i_{B_1}, i_{E_3}, i_{B_2}, v_o$.
- Find out the power dissipation of the TTL circuit for both (a) and (b).
- Find the maximum fanout of this TTL circuit for the case described in (a).
- If at least one input is low (0.1 V) and 2 loads are connected to the output find the new value for v_o .

Ans: a) $0.4 \text{ mA}, 1.36 \text{ mA}, 3.249 \text{ mA}, 0.0114 \text{ mA}, 3.431 \text{ mA}$

b) $0.867 \text{ mA}, 0.433 \text{ mA}, 0 \text{ mA}, 2.8 \text{ V}$

c) $12.36 \text{ mW}, 2.9478 \text{ mW}$

d) 56

e) 2.396 V