

Exercise 1

Implement the following logic function with- i) NMOS only ii) PMOS only iii) CMOS only

$$Y=(A+B)C$$

